

EE5803 - FPGA LAB

Assignment-1

Venkatesh Parvathala
EE22RESCH01005

January 15, 2022

Q. Reduce the following boolean expression to its simplest form using K-Map.

$$F(X, Y, Z, W) = \sum(0, 1, 2, 3, 4, 5, 10, 11, 14) \quad (1)$$

Sol. First we will build a Truth Table for the given expression as below,

X	Y	Z	W	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Table 1: The Truth Table

K-Map for the given expression as below

		ZW			
		00	01	11	10
XY	00	1	1	1	1
	01	1	1	0	0
	11	0	0	0	1
	10	0	0	1	1

The implicants in 0,1,4,5 gives us $\bar{X}\bar{Z}$

The implicants in 2,3,10,11 gives us $\bar{Y}Z$

The implicants in 10,14 gives us $XZ\bar{W}$

Combining all the above terms will give us

$$F(X, Y, Z, W) = \bar{X}\bar{Z} + \bar{Y}Z + XZ\bar{W} \quad (2)$$

In order to implement it using NAND gates, we will write the above SOP form as below

$$F(X, Y, Z, W) = \overline{(\bar{X}\bar{Z} + \bar{Y}Z + XZ\bar{W})} \quad (3)$$

$$F(X, Y, Z, W) = \overline{(\bar{X}\bar{Z}.\bar{Y}Z.XZ\bar{W})} \quad (4)$$

The above equation can be implemented using NAND gates and the corresponding code is available at `./assignment_1.c`